

Electrical Engineering



Electronics and Communication Engineering

Digital Electronics



Lecture No.-03

DAC & ADC



By- Chandan Gupta Sir



Topics to be Covered

DAC. Cont.


Questions discussion on DAC.

[Inverted Ladder]



Why inverted ladder in place normal ladder ?

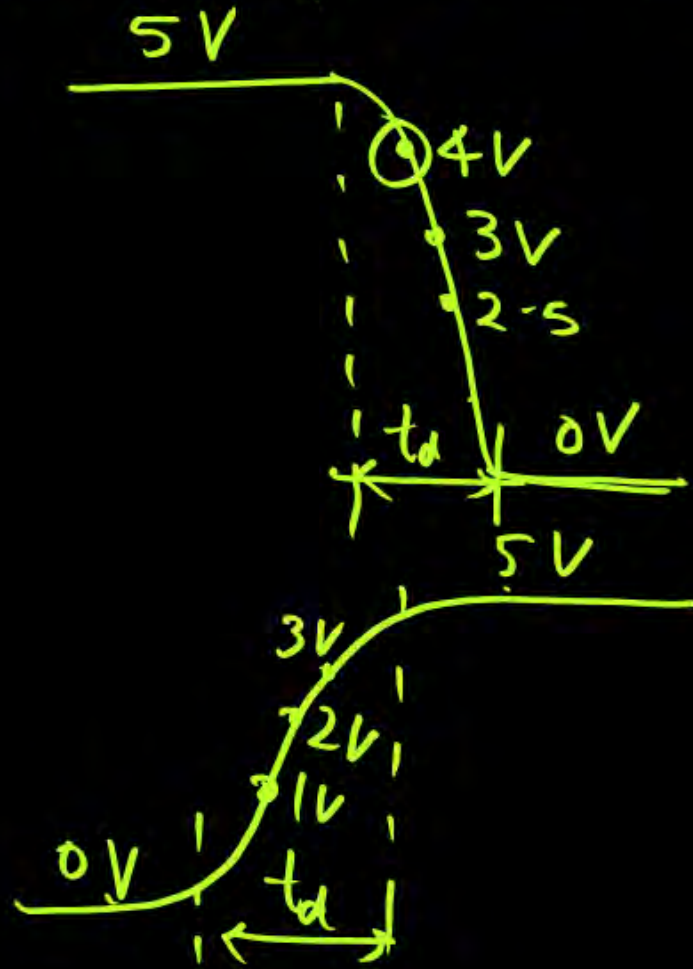- In Normal ladder when digital i/p changes, due to switching delay we get transient error in the o/p before getting the actual or steady state o/p. To remove this error we use inverted ladder.




$b_2 \rightarrow 5V \rightarrow 0V$
 $b_1 \rightarrow 0V \rightarrow 5V$
 $b_0 \rightarrow 5V \rightarrow 5V$

$b_2 \ b_1 \ b_0$
 $1 \ 0 \ 1 \rightarrow \frac{5}{8} \times 5 \text{ Vol}$
 $b_2 \rightarrow 5V$
 $b_1 \rightarrow 0V$
 $b_0 \rightarrow 5V$
 $\rightarrow \frac{25}{8} \times A$
 $0 \ 1 \ 1 \rightarrow \frac{5}{8} \times 3 = \frac{15}{8} \times A$

Circuit :

$n=3\text{bits}$

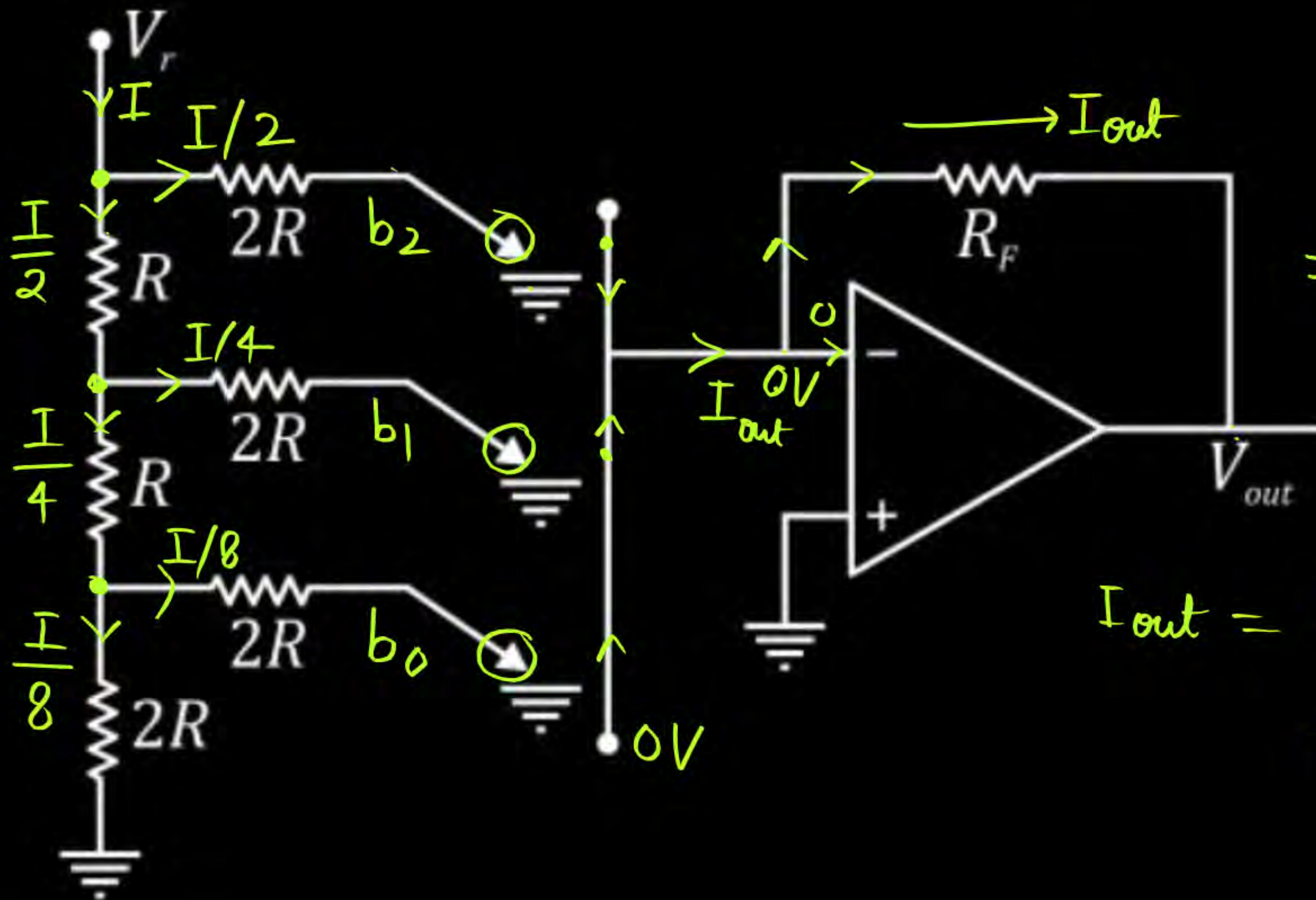

$$\Rightarrow \frac{0 - V_{out}}{R_F} = I_{out}$$

$$V_{out} = -I_{out} R_F$$

$$I_{out} = b_2 \cdot \frac{I}{2} + b_1 \cdot \frac{I}{4} + b_0 \cdot \frac{I}{8}$$

Working :

$$I_{out} = \frac{I}{8} \left[2^2 b_2 + 2^1 b_1 + 2^0 b_0 \right]$$

$$\frac{I}{2} = \frac{V_{in} - 0}{2R} \Rightarrow I = \frac{V_{in}}{R}$$

$$I_{out} = \frac{1}{R} \frac{V_{in}}{8} \left[\text{decimal equivalent of (IP digital data)} \right]$$

$$I_{out} = \frac{1}{R} \times \text{Resolution} \times \text{decimal equivalent of i/p digital data}$$

$$V_{out} = -\frac{R_F}{R} \times \text{Resolution} \times \text{decimal equivalent of i/p digital data}$$

$$\begin{aligned} \text{Resolution} \\ = \frac{V_{in}}{2^n} \end{aligned}$$

[Question]




A digital to analog converter circuit is as given below :

$b_2 b_1 b_0 \rightarrow n=3 \text{ bits}$

$1 \ 1 \ 0 \rightarrow (6)_{10}$

$V_R = 5 \text{ V}$

I.

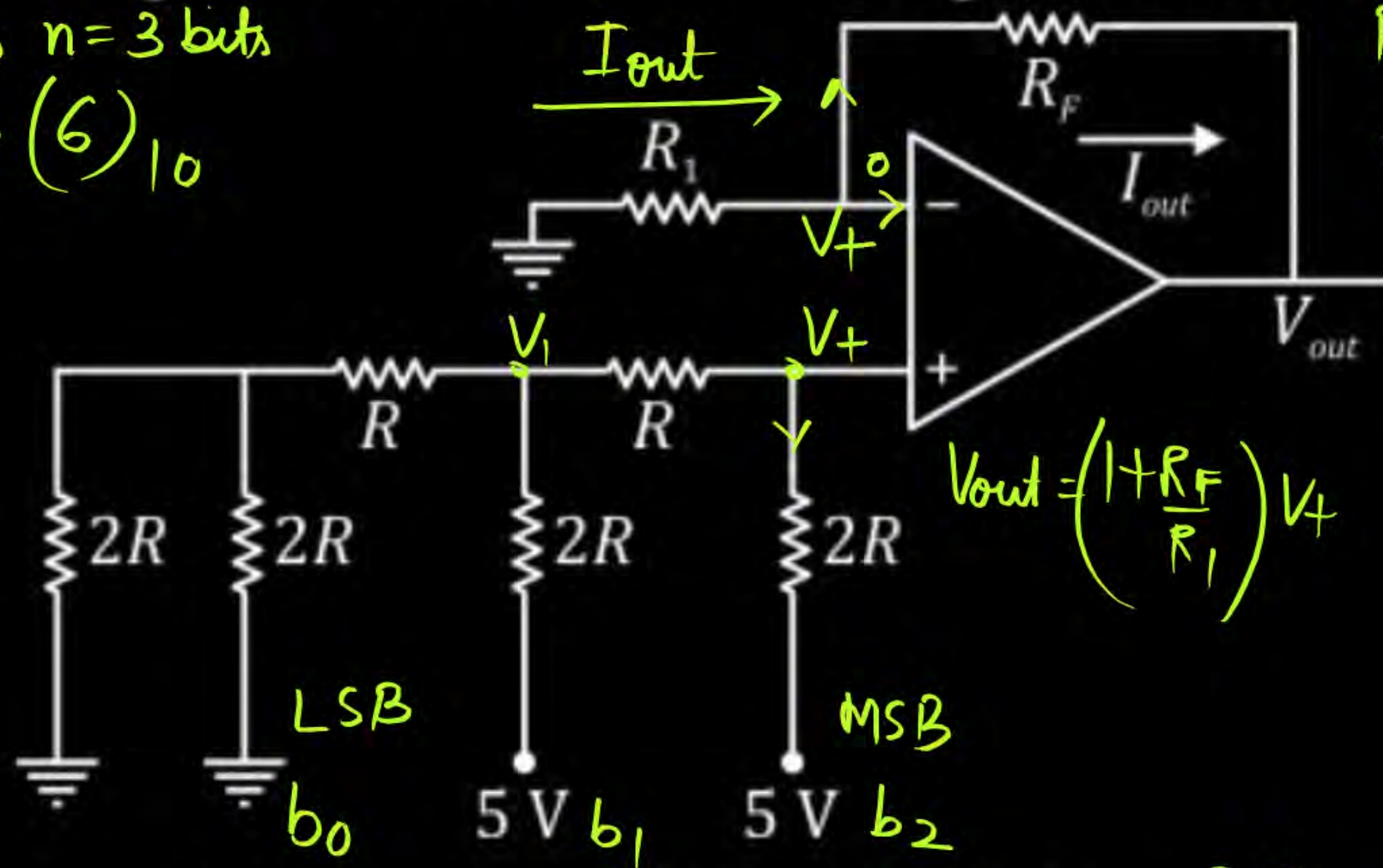

$$\text{Resolution} = \frac{V_R}{2^n} = \frac{5}{8} \text{ Volt}$$

$$V_+ = \text{Resolution} \times \text{decimal equivalent} \\ = \frac{5}{8} \times 6 = \frac{15}{4} \text{ V}$$

$$V_{out} = \left(1 + \frac{R_F}{R_1}\right) V_+$$

$$I_{out} = \frac{0 - V_+}{R_1} \\ = -\frac{15/4}{1.5} \\ = -\frac{5}{2} = -2.5 \text{ mA}$$

(a) Value of output current I_{out} if $R_1 = 1.5 \text{ k}\Omega$ -2.5 (mA).

(b) Value of output voltage V_{out} if $R_1 = 2 \text{ k}\Omega$ and $R_F = 3 \text{ k}\Omega$ 9.375 volts.

$$(b) \quad V_{out} = \left(1 + \frac{R_F}{R_1}\right) V_+ = \left(1 + \frac{3}{2}\right) \cdot \frac{15}{4} = \frac{5}{2} \times \frac{15}{4} = \frac{75}{8} \text{ Volt}$$

[Question]



A digital to analog converter circuit is as given below :


$$R = 1\text{ k}\Omega, 2R = 2\text{ k}\Omega$$

$n = 3$ bits

$b_2 b_1 b_0$

1 0 0

\downarrow
 $(4)_{10}$

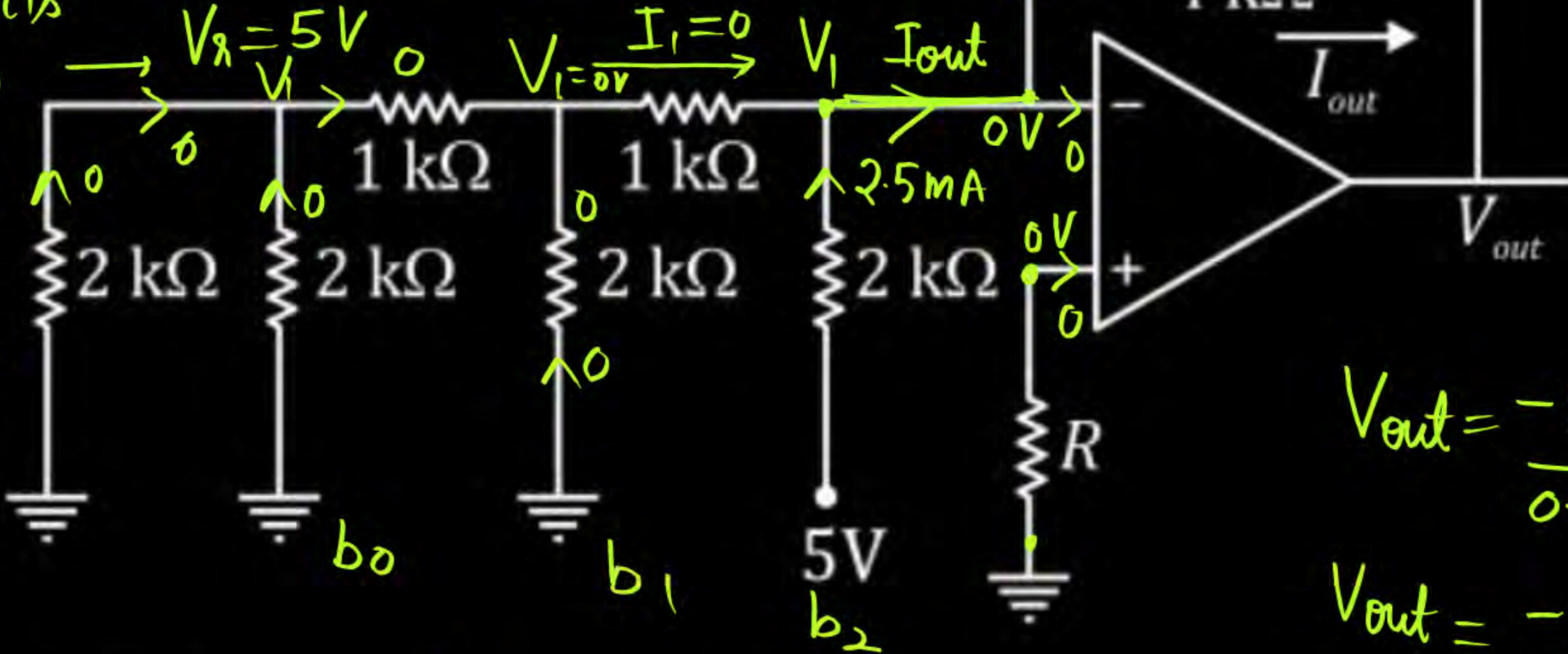

$$\begin{aligned} \text{Resolution} &= \frac{V_n}{2^n} \\ &= \frac{5\text{ V}}{2^3} \\ &= 5/8 \text{ Volt} \end{aligned}$$

$$V_{out} = -\frac{R_F}{0+R} \times \text{Resolution} \times \text{decimal equivalent}$$

$$V_{out} = -\frac{4}{1} \times \frac{5}{8} \times 4$$

$$= -10\text{ V}$$

$$I_{out} = \frac{0 - V_{out}}{R_F} = \frac{10}{4} = 2.5\text{ mA}$$


(a) Value of V_{out} is -10 volts.

(b) Value of I_{out} is 2.5 mA.

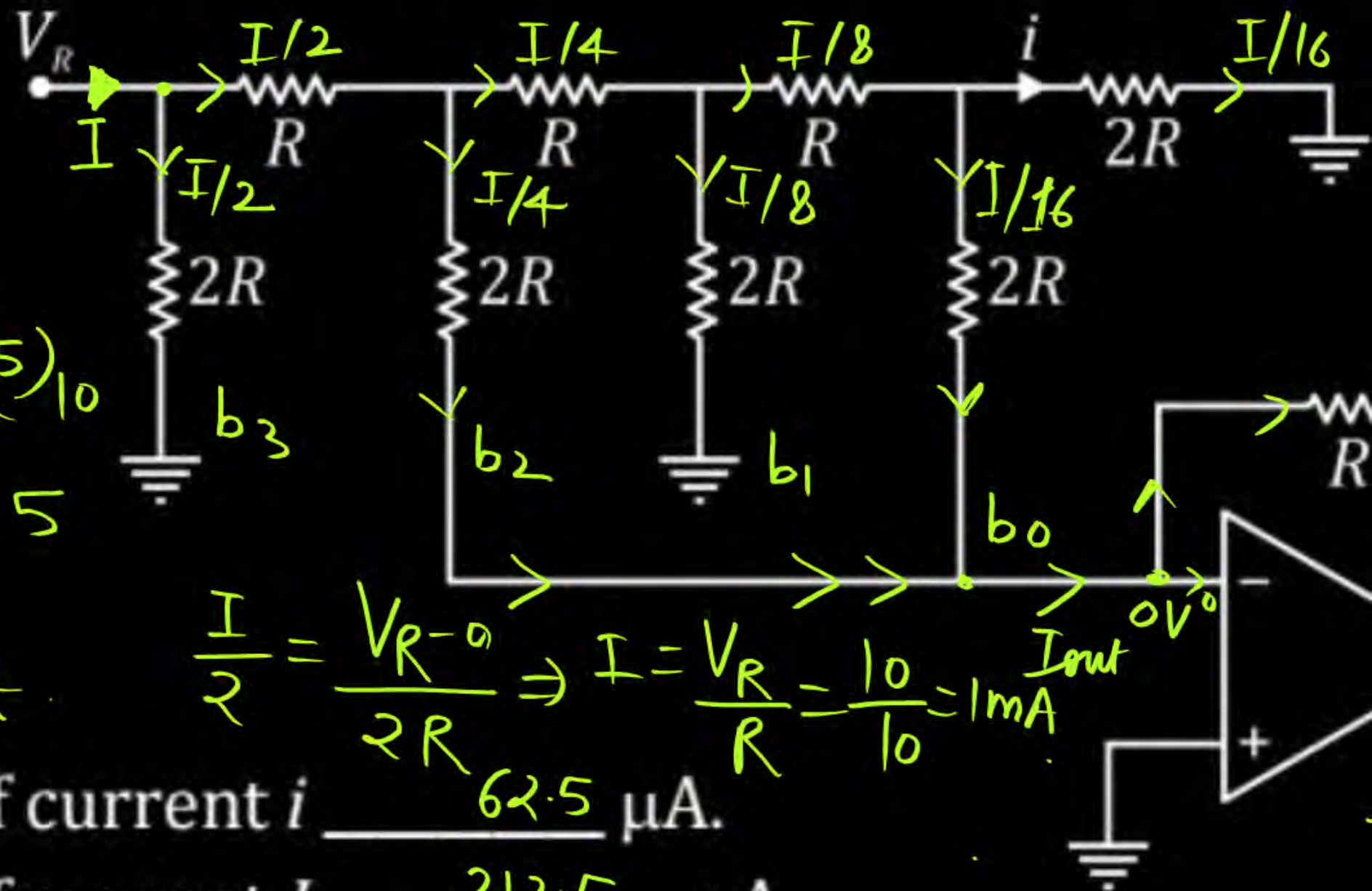[Question]



In digital to analog converter circuit shown in figure below $V_R = 10\text{ V}$ and $R = 10\text{ k}\Omega$.



$n = 4$ bits

$b_3 b_2 b_1 b_0$

$\Rightarrow 0101 = (5)_{10}$

$$V_{out} = -\frac{R}{R} \frac{10}{2^4} \times 5 = -50/16 \text{ Volt}$$

$$\frac{I}{2} = \frac{V_R - 0}{2R} \Rightarrow I = \frac{V_R}{R} = \frac{10}{10} = 1\text{mA}$$

$$i = I/16$$

$$= \frac{1}{16} \text{ mA}$$

$$= \frac{1000}{16} \mu\text{A} = 62.5 \mu\text{A}$$

The value of current i 62.5 μA .

The value of current I_{out} 312.5 μA .

The value of output voltage V_{out} -3.125 Volts.

$$I_{out} = \frac{I}{4} + \frac{I}{16} = \frac{5I}{16} = 5 \times 62.5$$

Thank you

GW
Soldiers!

