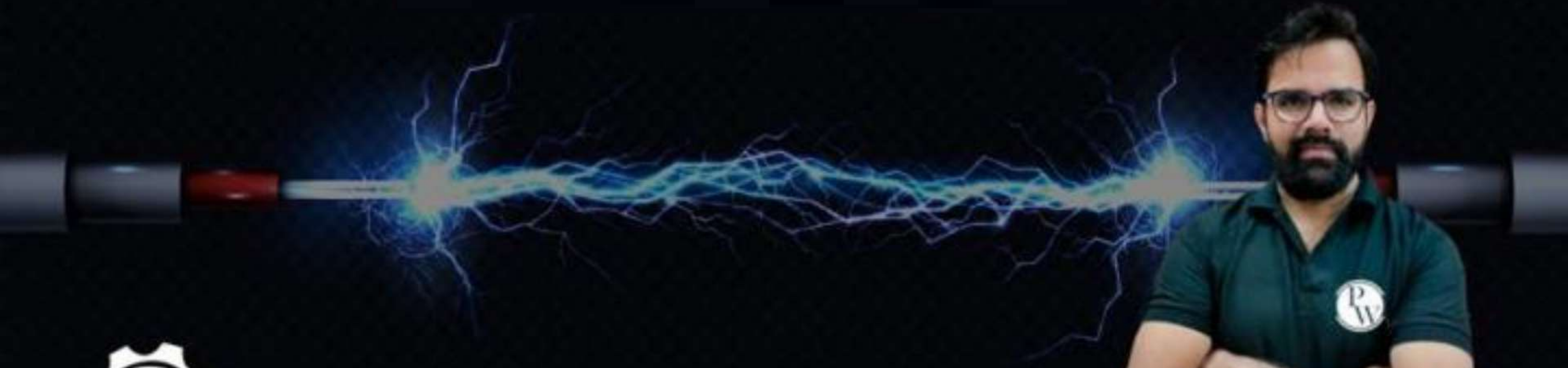


Electrical Engineering



Electronics and Communication Engineering

NETWORK THEORY



Lecture No. 10

Transient Analysis

By- Pankaj Shukla



Topics to be Covered

1. Question Discussion

2.

3.

4.


5.

6.

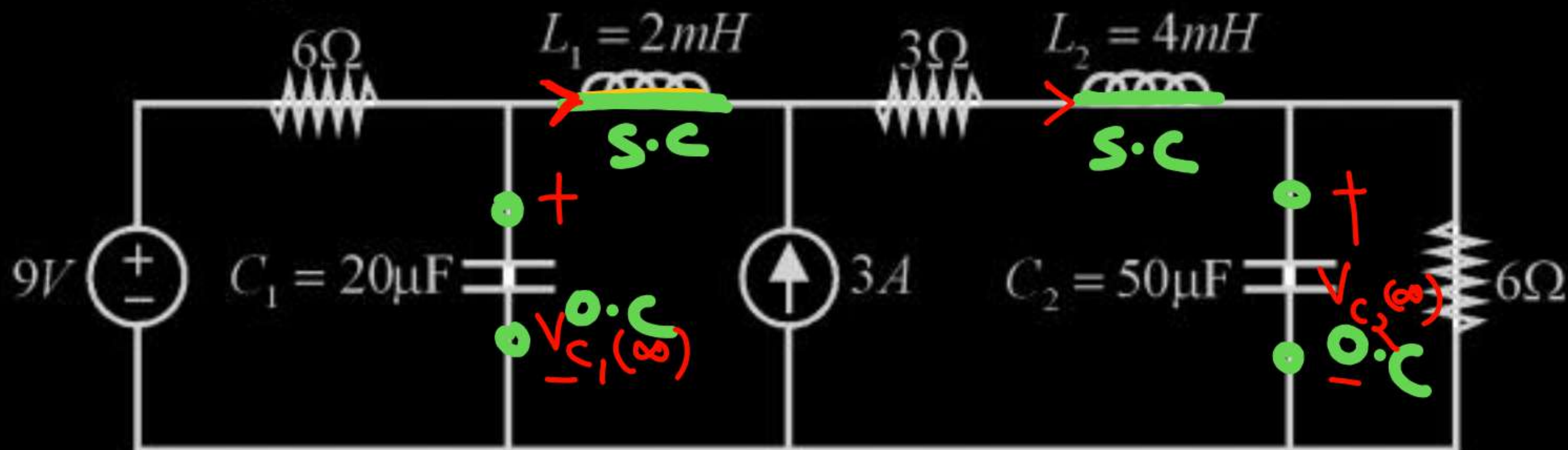Question




Find the energy stored in circuit shown below.



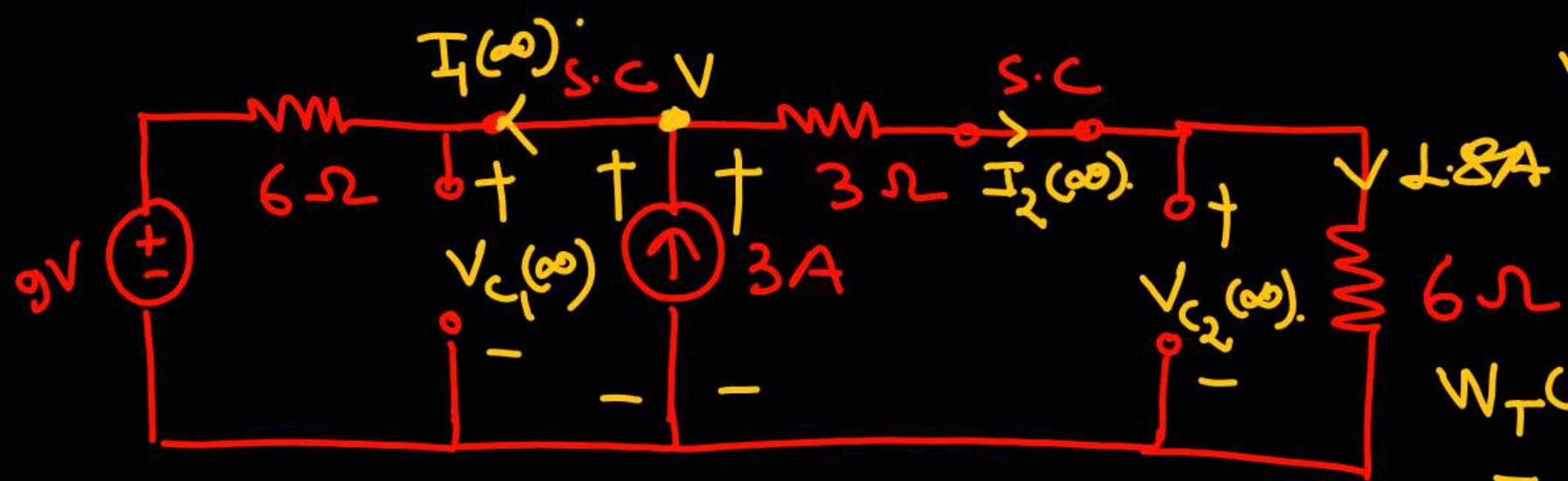- (A) 13.46mJ (B) 14.90mJ
(C) 12.28mJ (D) 16.17mJ

At Steady state.
 $L \rightarrow S.C$
 $C \rightarrow O.C$



$$V_{c2}(\infty) = (6 \times 1.8) = 10.8 \text{ V}$$

$$W_T(\infty) = (13.46 \text{ mJ})$$

$$= \frac{1}{2} \times 2 \times 10^{-3} \times (1.2)^2$$

Nodal $\rightarrow V \left(\frac{1}{6} + \frac{1}{9} \right) = 3 + \frac{9}{6}$

$$V = 16.24 \text{ V} = V_{c1}(\infty)$$

$$I_2(\infty) = \frac{V}{9} = \left(\frac{16.24}{9} \right) = (1.8 \text{ A})$$

$$I_1(\infty) = 3 - I_2(\infty) = 3 - 1.8 = (1.2 \text{ A})$$

$$+ \frac{1}{2} \times 4 \times 10^{-3} \times (1.8)^2$$

$$+ \frac{1}{2} \times 20 \times 10^{-6} \times (16.24)^2$$

$$+ \frac{1}{2} \times 50 \times 10^{-6} \times (10.8)^2$$



Question

Dr. W. Hefegram




The three inductors in the circuit in figure are connected across the terminals of a black box at $t = 0$. The resulting voltage for $t > 0$ is known to be

$$v_o = 2000e^{-100t} \text{ V.}$$

If $i_1(0) = -6 \text{ A}$ and $i_2(0) = 1 \text{ A}$, find

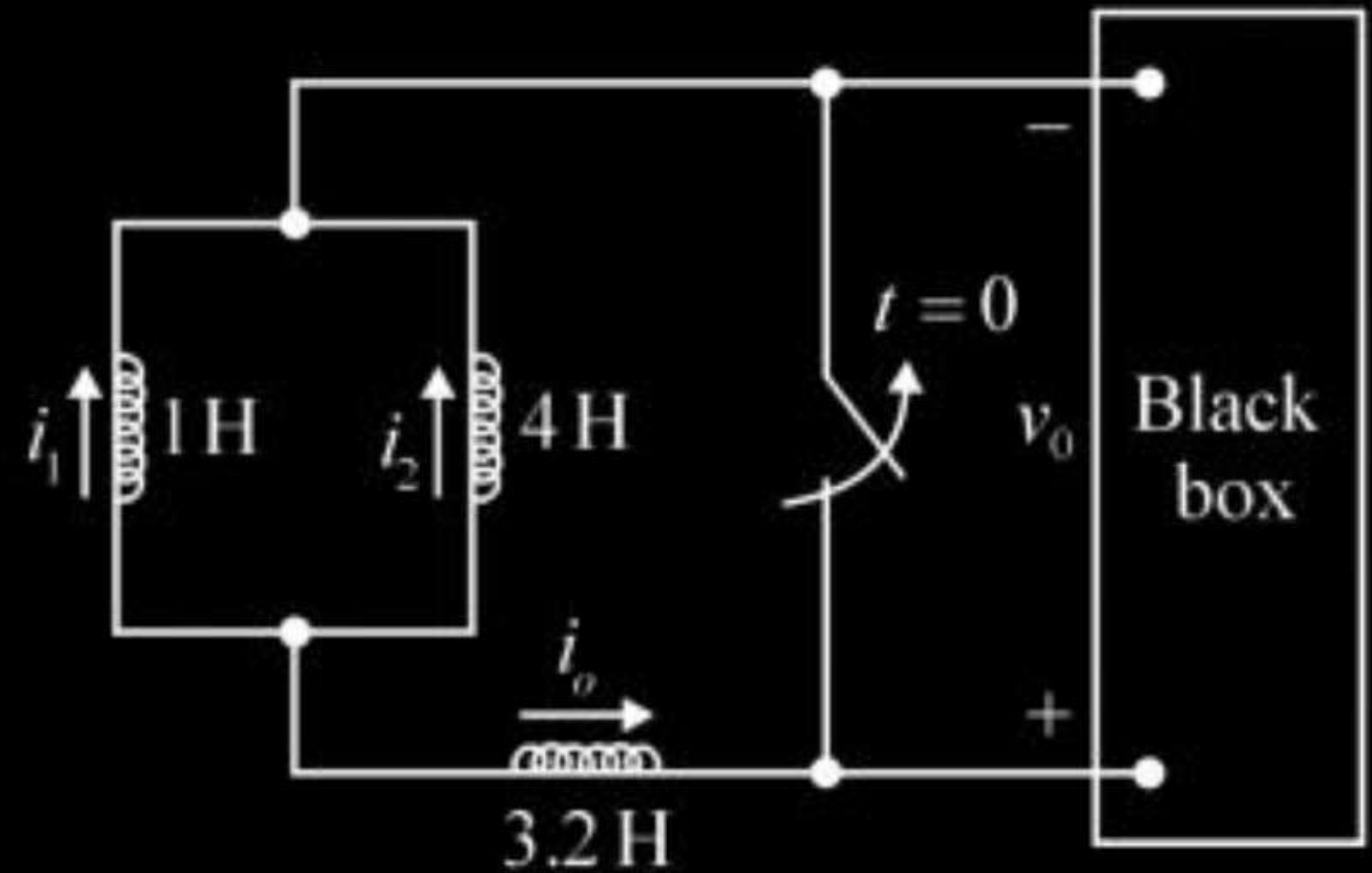- (a) $i_o(0)$;
- (b) $i_o(t), t \geq 0$;
- (c) $i_1(t), t \geq 0$;
- (d) $i_2(t), t \geq 0$;
- (e) The initial energy stored in the three inductors;
- (f) The total energy delivered to the black box; and
- (g) The energy trapped in the ideal inductors.



Question

The four capacitors in the circuit in figure are connected across the terminals of a black box at $t = 0$. The resulting current i_b for $t > 0$ is known to be


$$i_b = -5e^{-50t} \text{ mA.}$$




If $v_a(0) = -20 \text{ V}$, $v_c(0) = -30 \text{ V}$, and $v_d(0) = 250 \text{ V}$, find the following for $t \geq 0$:

- (a) $v_b(t)$, (b) $v_a(t)$, (c) $v_c(t)$, (d) $v_d(t)$,
(e) $i_1(t)$ and (f) $i_2(t)$.

For the circuit in figure calculate

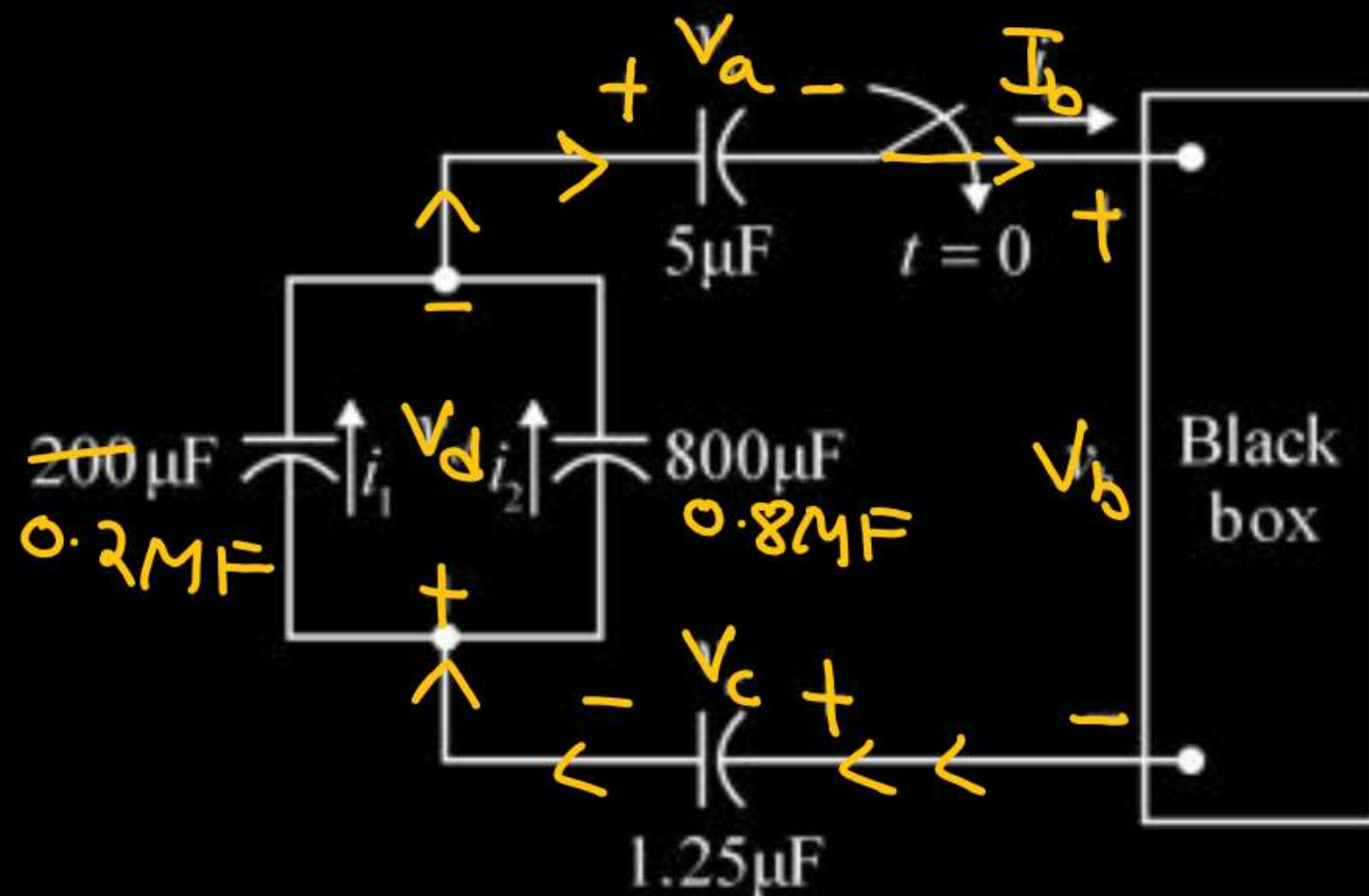- (a) The initial energy stored in the capacitors;
(b) The final energy stored in the capacitors;
(c) The total energy delivered to the black box;
(d) The percentage of the initial energy stored that is delivered to the black box; and
(e) The time in milliseconds, it takes to deliver 7.5 mJ to the black box.



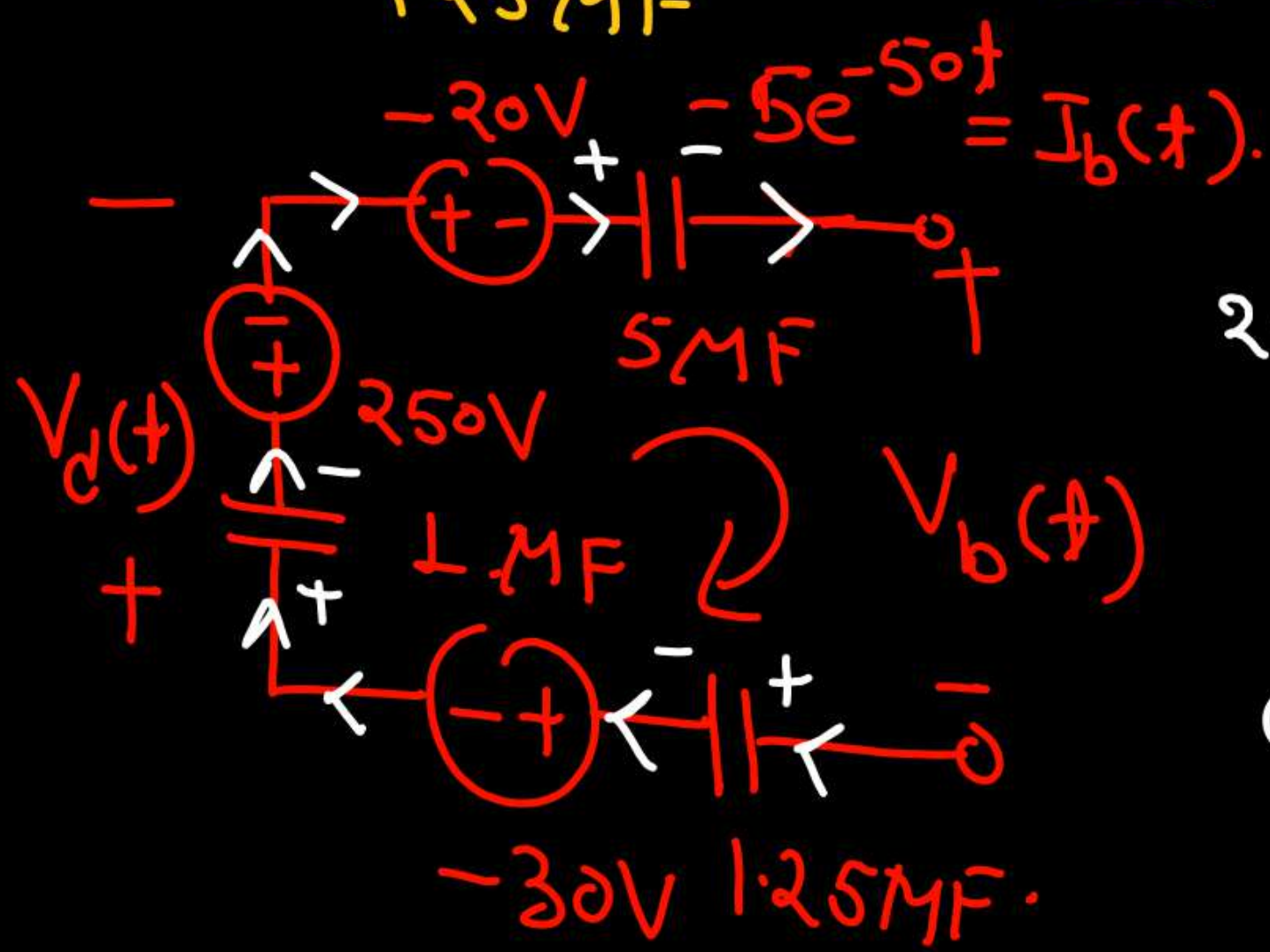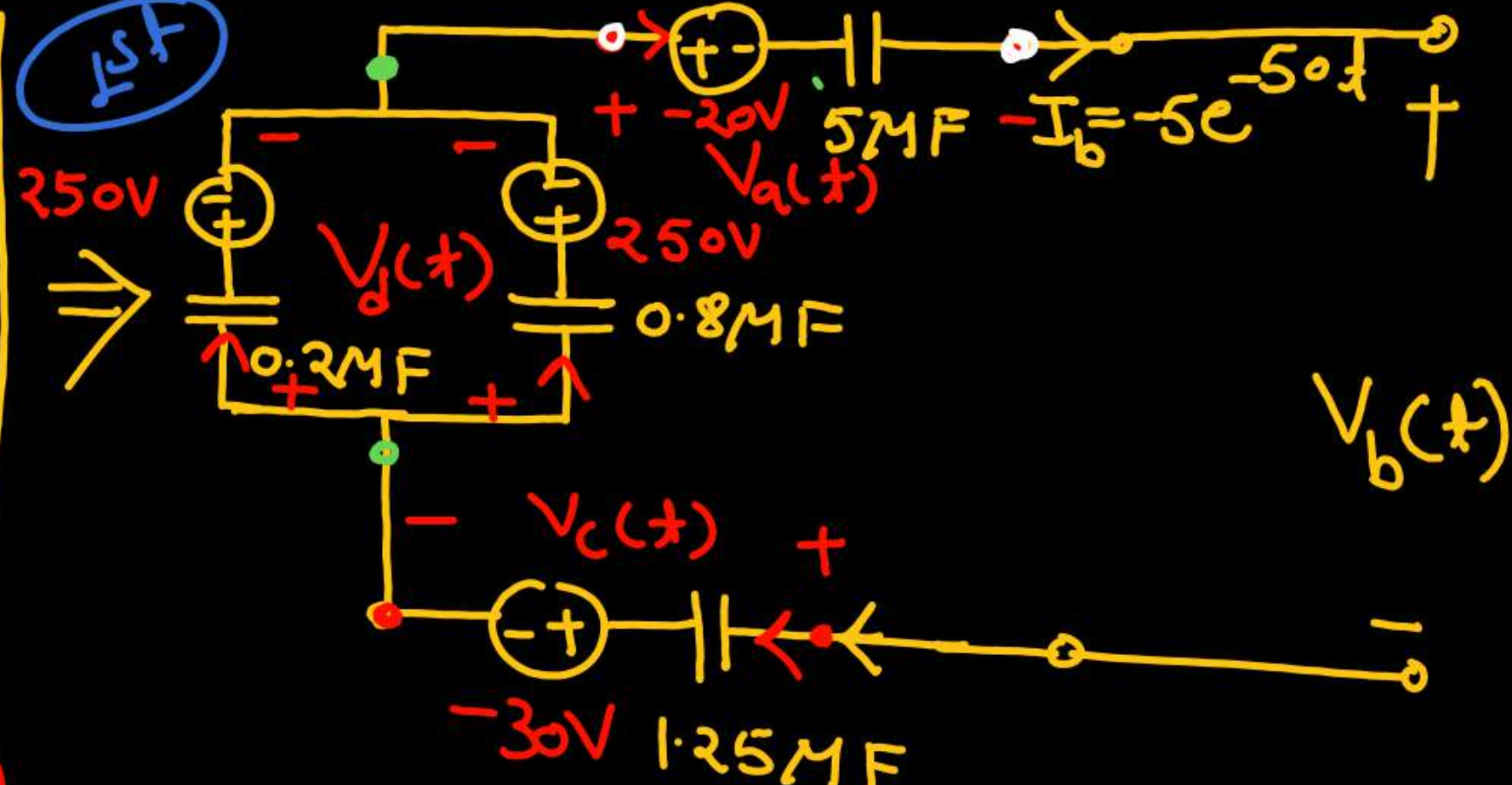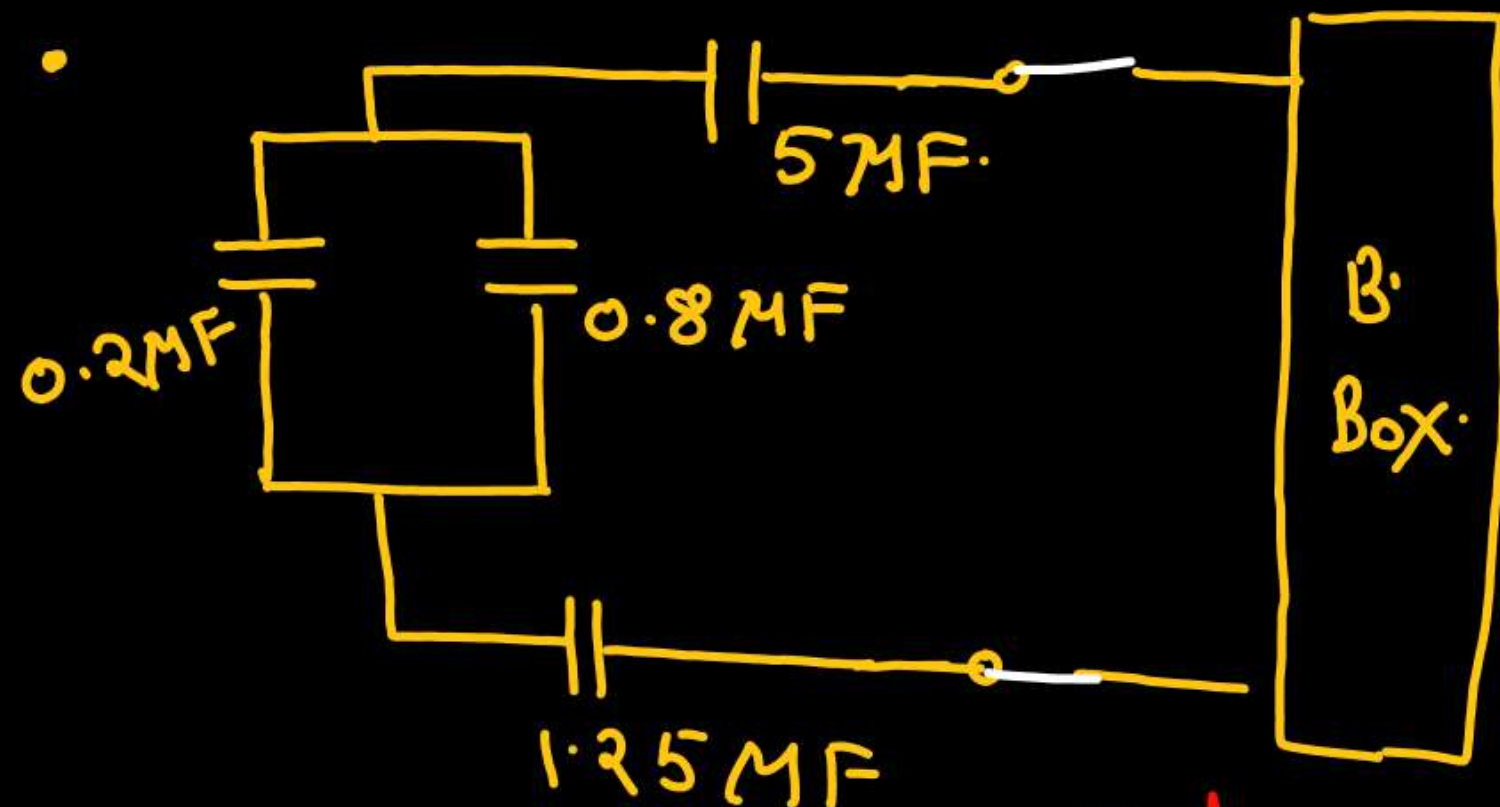

$$250 - 20 - 30 + \frac{1}{C_{eq}} \int I_b(t) dt = -V_b(t)$$

$$\frac{1}{C_{eq}} = \frac{1}{1.25} + \frac{1}{1} + \frac{1}{5} = 2$$

$$C_{eq} = \frac{1}{2} = 0.5\text{MF}$$

$$250 - 20 - 30 + \frac{1}{0.5 \times 10^{-6}} \times \int_0^t (-5e^{-50t} \times 10^{-3}) \cdot dt = v_b(t).$$


②

$$\checkmark \boxed{v_b(t) = -20e^{-50t} \text{ V.}}$$


• $v_a(t)$, $v_c(t)$, $v_d(t)$.

③ $v_a(t) = -20 + \frac{1}{5 \times 10^{-6}} \int_0^t (-5e^{-50t} \times 10^{-3}) dt = (20e^{-50t} - 40)$

$$v_a(\infty) = -40 \text{ V}$$

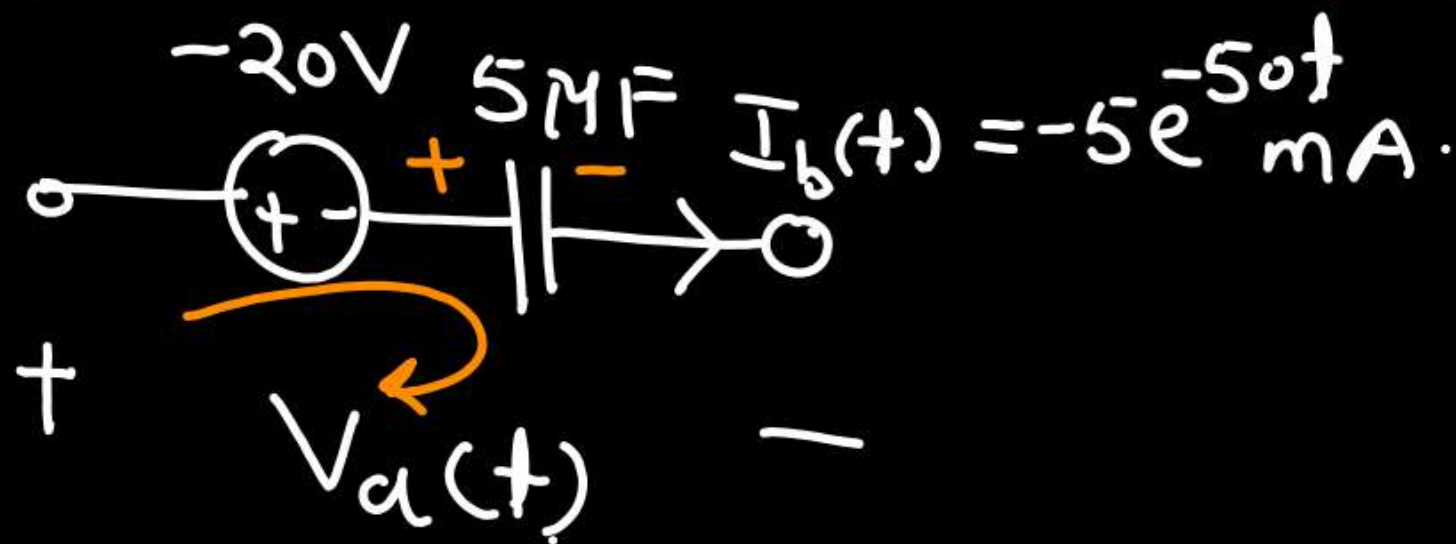

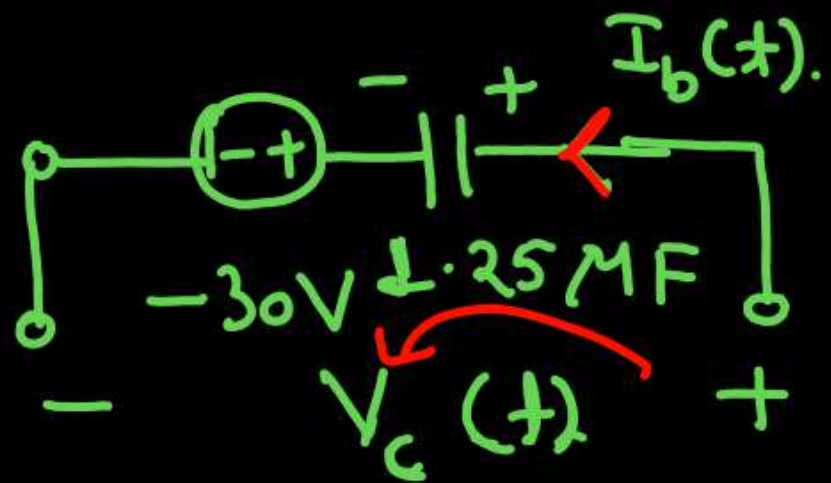
$$\textcircled{4} V_C(t) = -30 + \frac{1}{1.25 \times 10^{-6}} \int_0^t (-5 \times 10^{-3}) e^{-50t} dt.$$



$$\left[V_C(t) = 80 e^{-50t} - 110 \text{ V} \right]$$

$$(V_C(\infty) = -110 \text{ V})$$

$$\textcircled{5} V_d(t) = ?$$

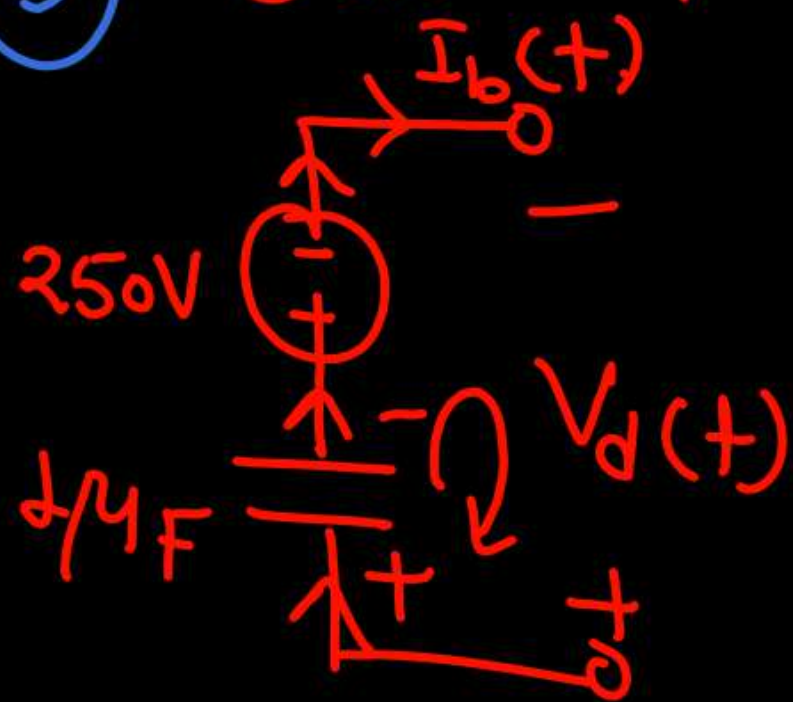

$$V_d(t) = 250 + \frac{1}{4 \times 10^{-6}} \int_0^t (-5 \times 10^{-3} e^{-50t}) dt.$$

$$\left[V_d(t) = (100 e^{-50t} + 150) \text{ volt} \right]$$

$$V_d(\infty) = 150 \text{ V}$$

$$\textcircled{6} \quad W_T(0^+) = \frac{1}{2} \times 5 \times 10^{-6} \times (-20)^2 + \frac{1}{2} \times 1.25 \times 10^{-6} \times (-30)^2$$

$$+ \left[\frac{1}{2} \times 0.2 \times 10^{-6} \times (250)^2 + \frac{1}{2} \times 0.8 \times 10^{-6} \times (250)^2 \right]$$

$$= (32812.5 \text{ } \mu\text{Joule})$$

$$\textcircled{7} \quad W_T(\infty) = W_{T(\text{trapped})} = \frac{1}{2} \times 5 \times 10^{-6} \times (-40)^2 + \frac{1}{2} \times 1.25 \times 10^{-6} \times (-110)^2$$

$$+ \frac{1}{2} \times 1 \times 10^{-6} \times (150)^2$$

$$= 22812.5 \text{ } \mu\text{Joule}$$

$$\textcircled{8} \quad W_{\text{Delivered to the B. Black box}} = W_{\text{B.B. (Absorbing)}}$$

$$= W_T(0) - W_T(\infty) = (10,000 \text{ } \mu\text{J})$$

- What Percentage of initial energy delivered to the B.B. during reaching to S.S.

$$\frac{W_{B.B.}}{W_T(0)} = \frac{10,000}{32812.5} \times 100 = (30.47 \%)$$

Question





At $t = 0$, a series-connected capacitor and inductor are placed across the terminals of a black box, as shown in figure. For $t > 0$, it is known that

$$i_o = 200e^{-800t} - 40e^{-200t} \text{ mA} \rightarrow (t > 0) \rightarrow t \geq 0$$

If $v_c(0) = 5 \text{ V}$ find v_o for $t \geq 0$.

$$i_L(0^-) = i_L(0^+) = 0 \text{ A}$$

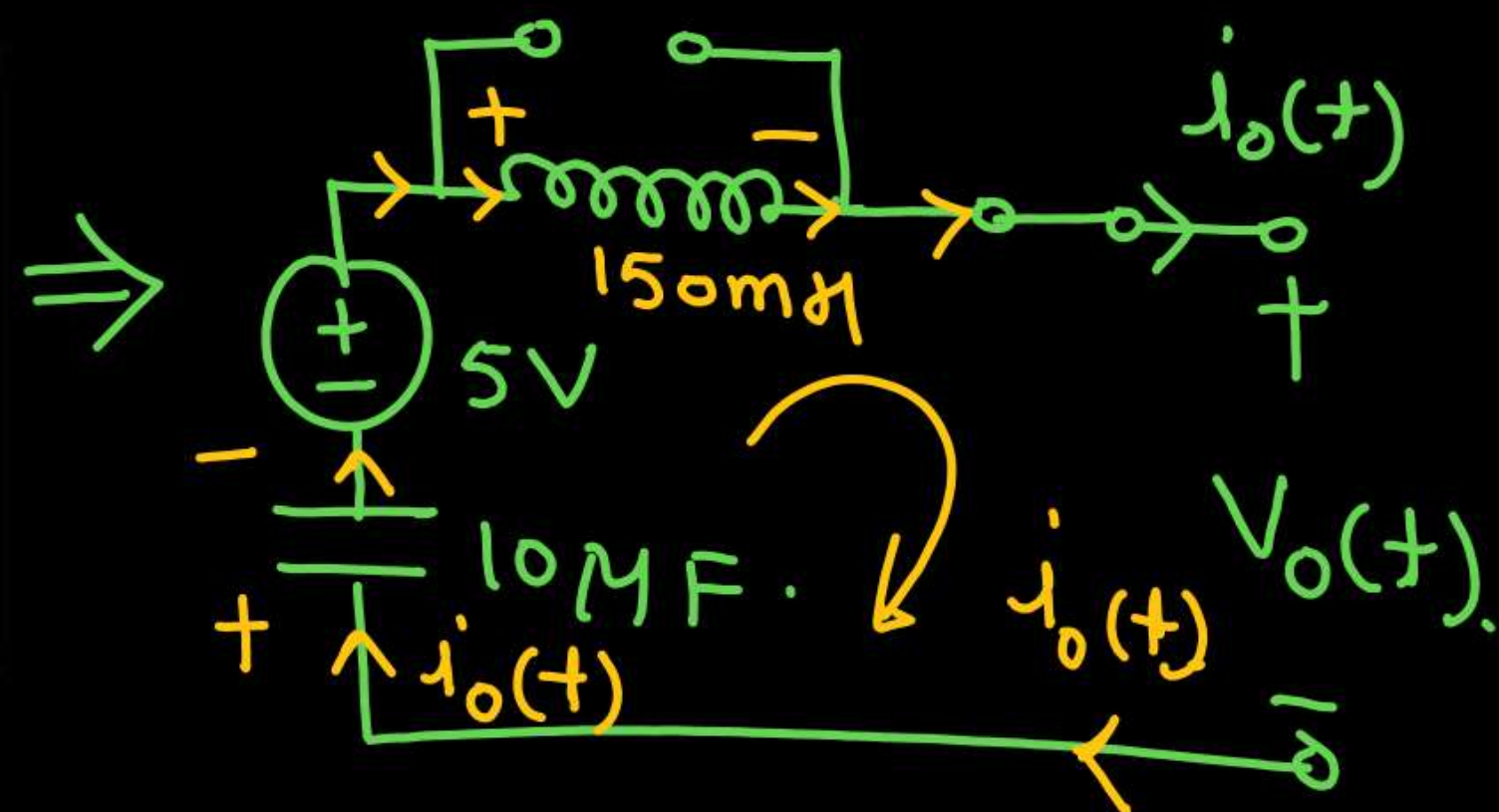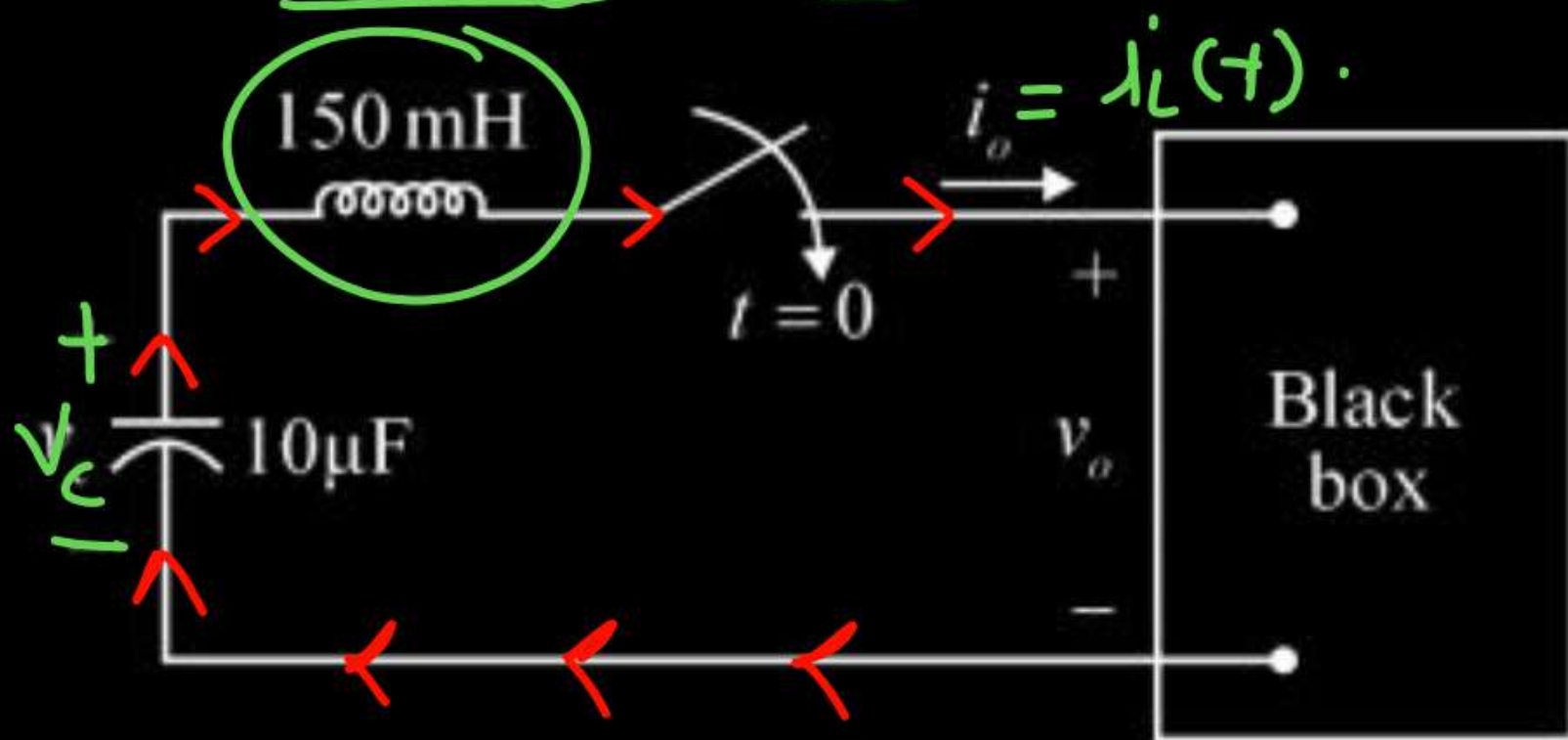

$$V_o(t) + \frac{1}{10 \times 10^{-6}} \int i_o(t) dt + 150 \times 10^3 \frac{di_o}{dt} = 5$$

$$V_o(t) = 5 - \frac{10^{-3}}{10 \times 10^{-6}} \int_0^t (2\omega e^{-8\omega t} - 40 e^{-2\omega t}) dt - 150 \times 10^3 \times 10^{-3} \times \left(\frac{d}{dt} (2\omega e^{-8\omega t} - 40 e^{-2\omega t}) \right)$$

$$V_o(t) = 5 - \frac{1}{10 \times 10^3} \left[\left(\frac{2\omega e^{-8\omega t}}{-8\omega} \right)_0^t + \left[\frac{40 e^{-2\omega t}}{200} \right]_0^t \right] - 150 \times 10^{-6} \times \left[2\omega e^{-8\omega t} \times (-8\omega) - 40 e^{-2\omega t} \times (-2\omega) \right]$$

1st

$$V_o(t) = (49 e^{-8\omega t} - 21.2 e^{-2\omega t}) (\text{Volt})$$


(2nd) $V_L(t) = L \frac{di_o(t)}{dt}$

$$= 150 \times 10^{-3} \frac{d}{dt} [0.2e^{-8\omega t} - 0.04e^{-2\omega t}]$$

$$V_L(t) = 150 \times 10^{-3} [0.2e^{-8\omega t} \times (-8\omega) - 0.04e^{-2\omega t} \times (-2\omega)]$$

(3rd)

$$V_C(t) = ?$$

$V_C(t) = 5 - \frac{1}{C} \int_0^t i_o(t) dt$

 h.w

$$\textcircled{4} \quad \underline{\underline{W_T(0)}} = \underbrace{\frac{1}{2} L \times I_L(0)^2}_{0\text{J}} + \underbrace{\frac{1}{2} \times C \times V_C(0)^2}_{\substack{\downarrow \\ 5\text{V}}} = (125 \mu\text{joule})$$

$$\left[\frac{1}{2} \times 10 \times 10^{-6} \times (25) \right]$$

$$\textcircled{5} \quad \underline{\underline{W_T(\infty)}} = \underbrace{\frac{1}{2} \times L \times i_L(\infty)^2}_{0\text{J}} + \underbrace{\frac{1}{2} \times C \times V_C(\infty)^2}_{\downarrow}$$

$$\textcircled{6} \quad \underline{\underline{\text{Energy delivered to B.B}}} = W_T(0) - W_T(\infty)$$

Question

Beautiful:

(2 minute)



The two switches shown in the circuit in Fig. operate simultaneously. Prior to $t = 0$ each switch has been in its indicated position for a long time. At $t = 0$ the two switches move instantaneously to their new positions. Find

(a) $v_o(t), t \geq 0^+$


(b) $i_o(t), t \geq 0$

It is a first order circuit.


$$I_L(t) = I_L(\infty) + [I_L(0^+) - I_L(\infty)]e^{-t/\tau}$$

\downarrow \downarrow
0A 0A

$$I_L(t) = I_L(0^+)e^{-t/\tau}$$

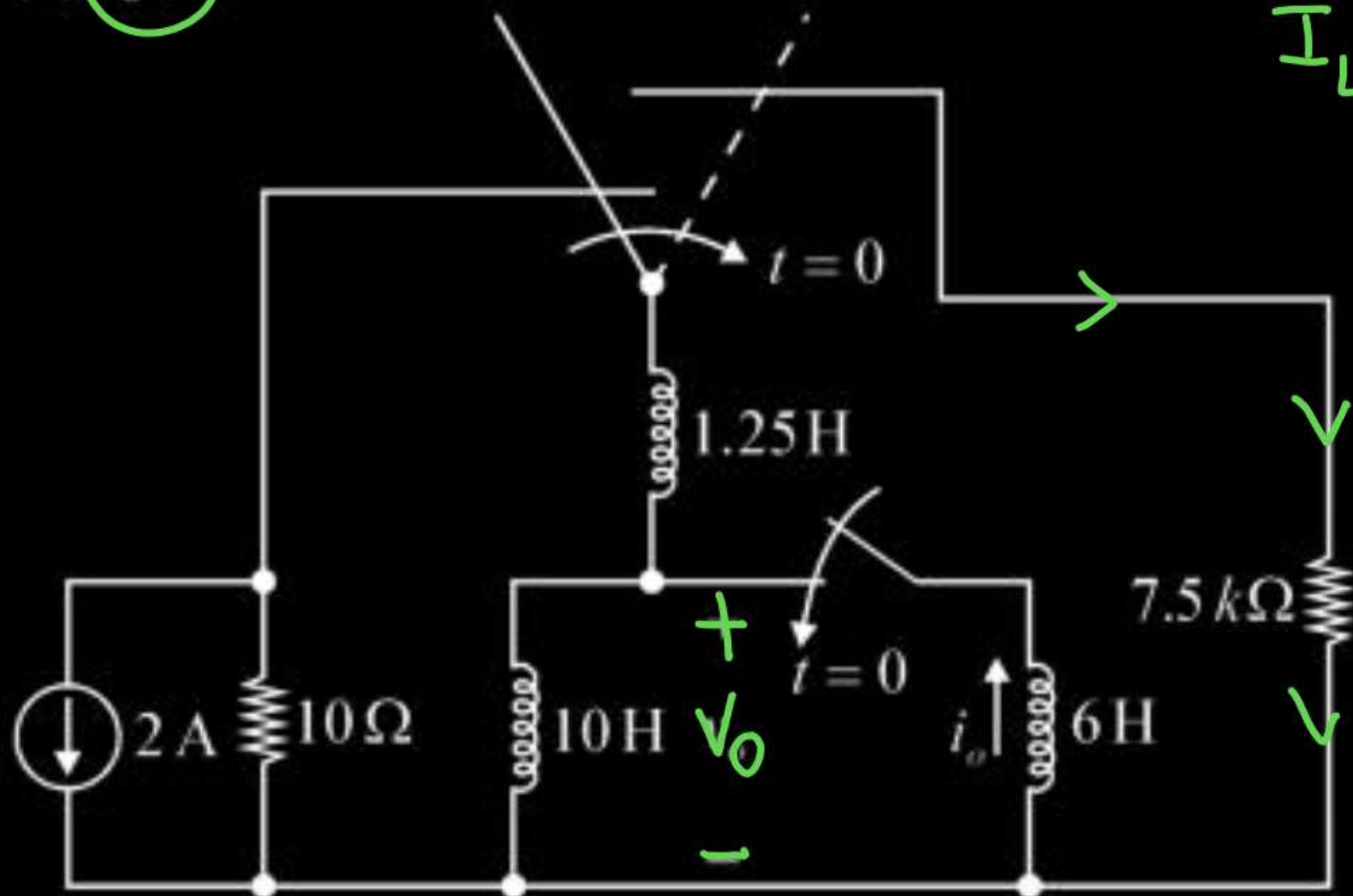

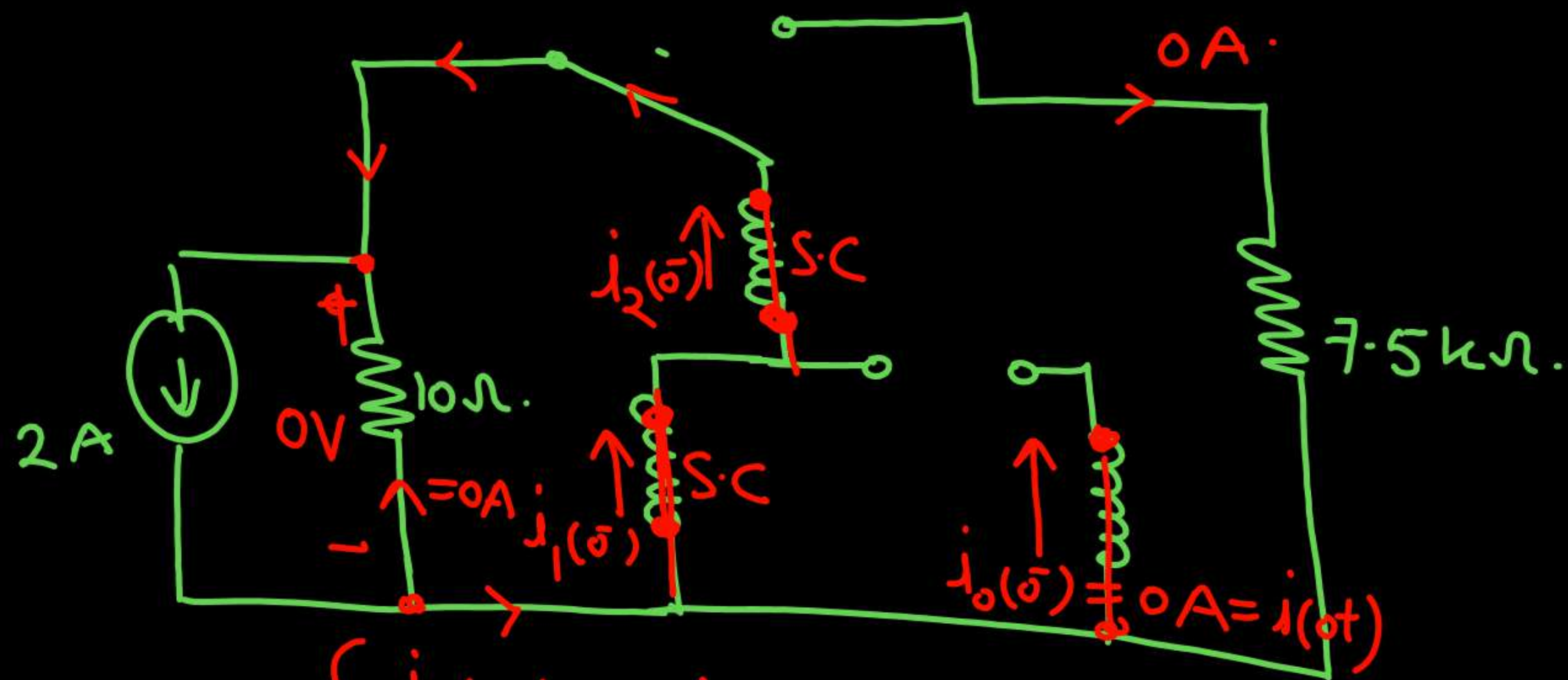- switching instant $\rightarrow t=0$.
- case-I $t < 0 \rightarrow t=0^-$ $L \rightarrow S.C \rightarrow (S.S)$.






$$\begin{cases} i_1(0^-) = i_2(0^-) = 2A \\ i_1(0^+) = i_2(0^+) = 2A \end{cases}$$

Case-II ($t > 0$)



(i) $t = \infty, i_1(\infty), i_2(\infty), i_o(\infty) = 0A$.

(ii) $t > 0 \rightarrow$

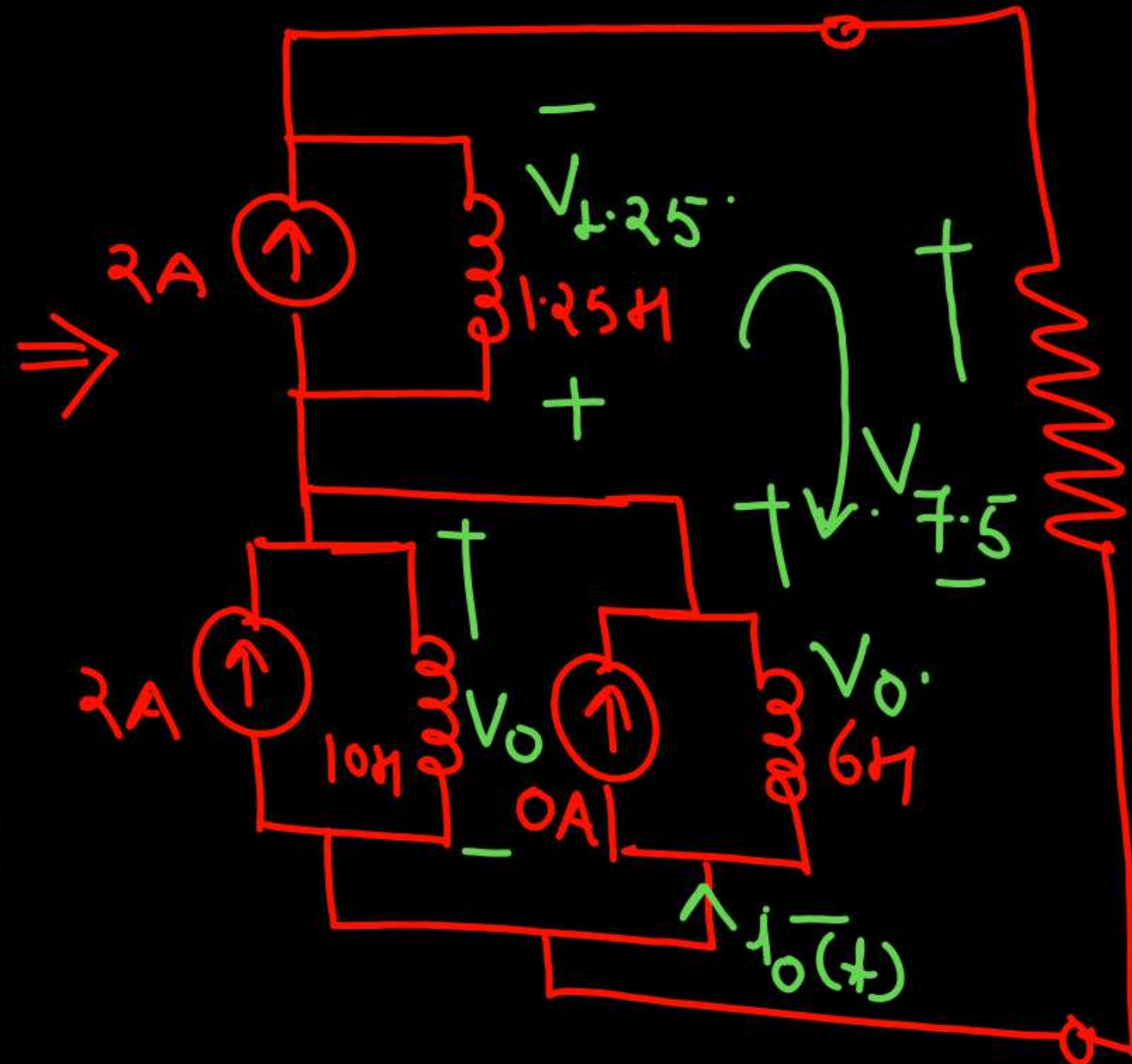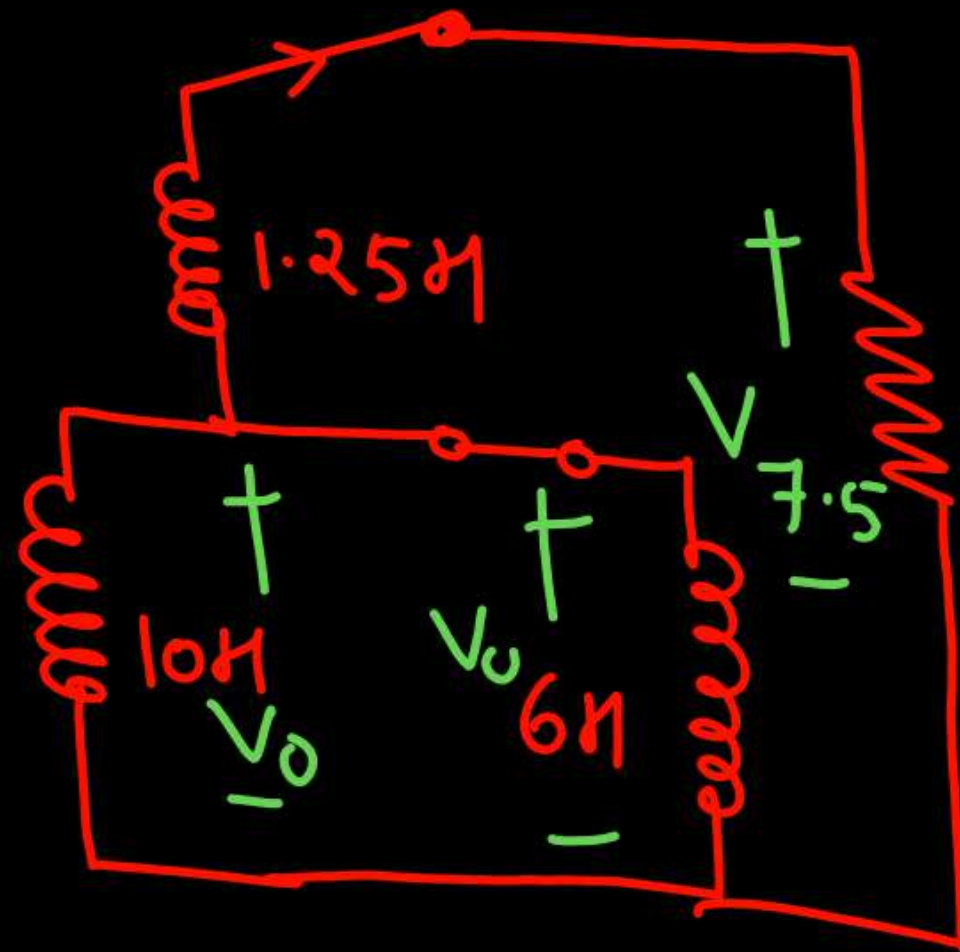

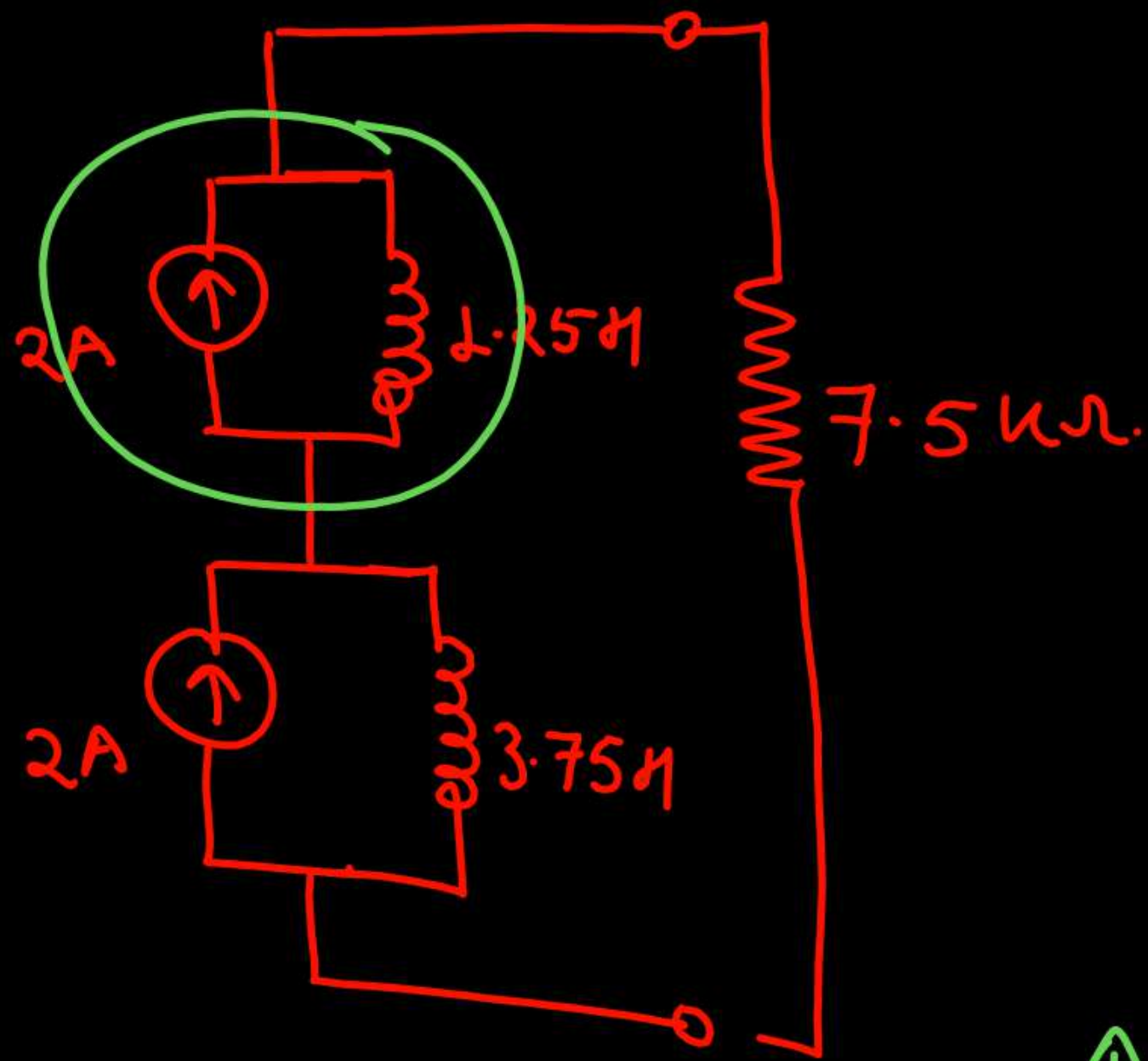

$$\tau = \left(\frac{5}{7.5k} \right)$$

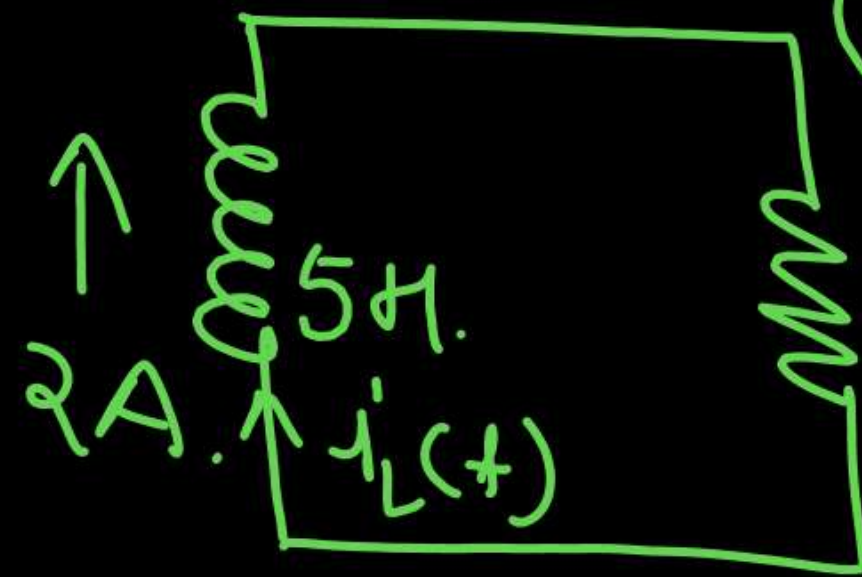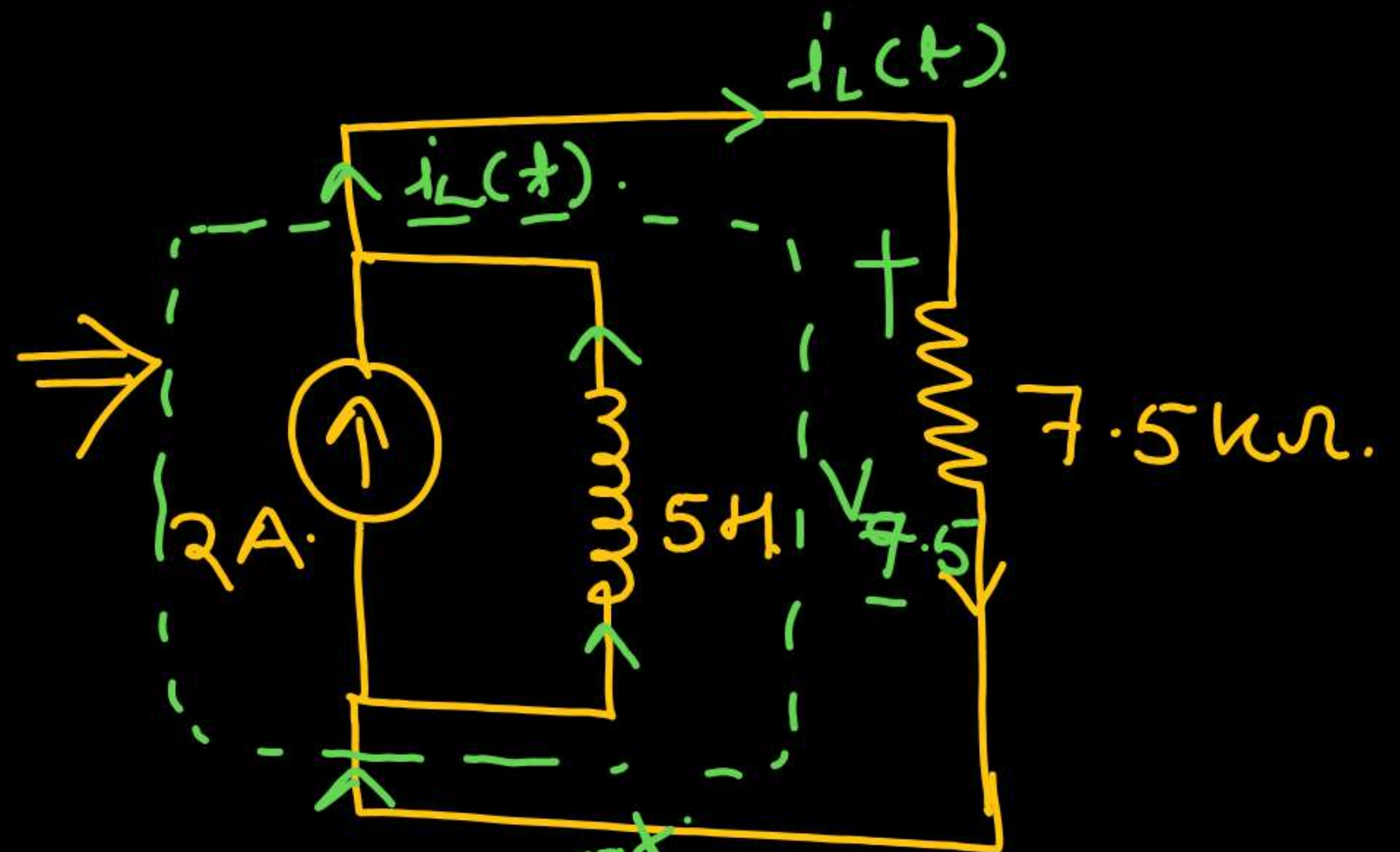

$$i_L(t) = 2 \times e^{-t/\tau} = (2e^{-1500t})$$

- Find the current in 1.25 H inductor for $t \geq 0$.

$$i_{1.25}(t) = i_L(t) = (2e^{-1500t})$$

- Find the voltage across ($7.5\text{ k}\Omega$)

$$V_{7.5}(t) = (2 \times e^{-1500t} \times 7.5 \times 10^3)$$

- Find the $V_o(t) = ?$


$$\begin{aligned} V_{1.25} &= 1.25 \cdot \frac{d}{dt} (2e^{-1500t}) = 1.25 \times 2 e^{-1500t} \times (-1500) \\ &= -3750 e^{-1500t}. \end{aligned}$$

- $$V_o(t) = V_{1.25}(t) + V_{7.5}(t)$$

$$= -3750e^{-15\omega t} + 15000e^{-15\omega t}$$

$$V_o(t) = 11.25e^{-15\omega t} \text{ kVolt.}$$

- Find the $i_o(t)$.

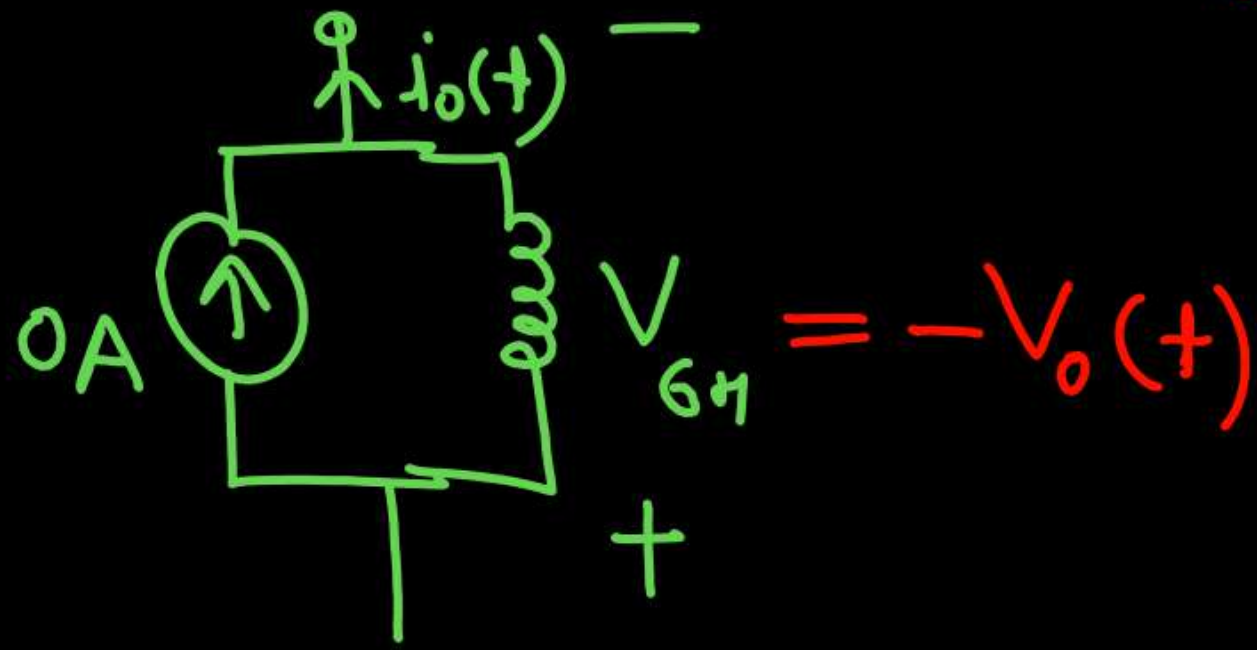

$$i_o(t) = \frac{1}{6} \int_0^t V_{6H} \cdot dt$$

$$= \left[-\frac{1}{6} \int_0^t 11.25 \times 10^3 e^{-15\omega t} \right]$$

Thank you

GW
Soldiers !

